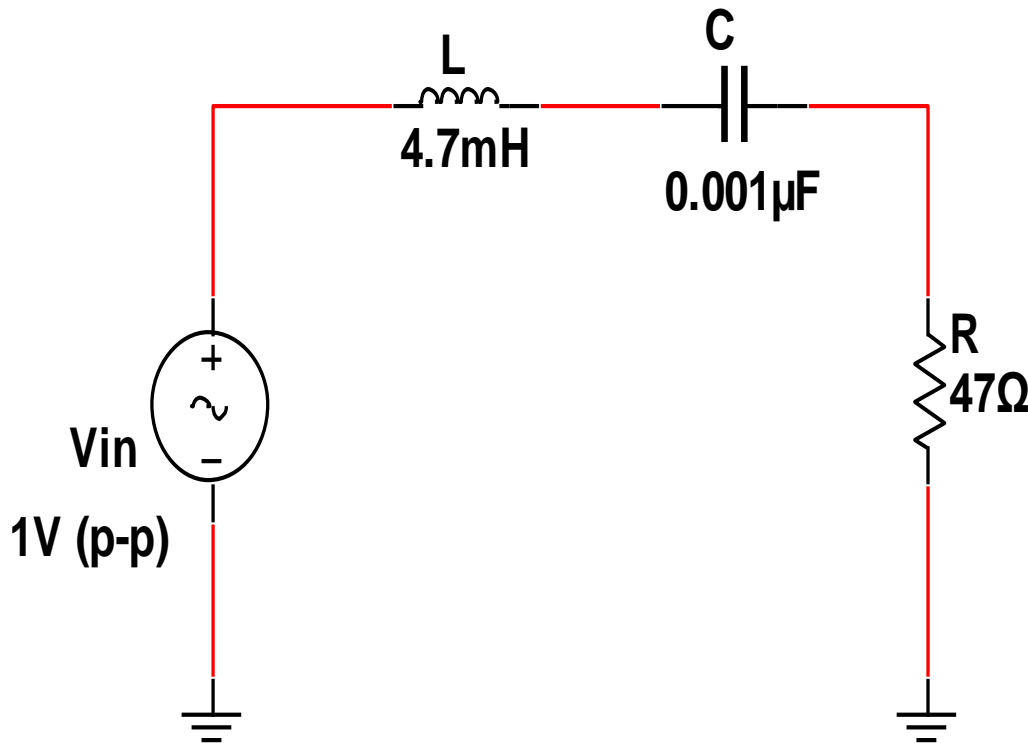


Series and Parallel Resonance

Series Resonant circuit



$$f_r = ?$$

$$V_C = ?$$

$$X_C = ?$$

$$V_L = ?$$

$$X_L = ?$$

$$Q = ?$$

$$I_T = ?$$

$$\Delta f = ?$$

$$\Theta = ?$$

Find f_r

$$\begin{aligned} \bullet f_r &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{6.28\sqrt{(4.7 \times 10^{-3})(0.001 \times 10^{-6})}} = \\ &= \frac{1}{6.28\sqrt{4.7 \times 10^{-12}}} = \frac{1}{1.362 \times 10^{-5}} = 73.412 \text{kHz} \end{aligned}$$

Find reactances

- $X_L = 2\pi fL = (6.28)(73.142 \times 10^3)(4.7 \times 10^{-6}) = 2.168 \text{ k}\Omega$

- $X_C = \frac{1}{2\pi fC} = \frac{1}{(6.28)(73.142 \times 10^3)(0.001 \times 10^{-6})} = \frac{1}{4.613 \times 10^{-4}} = 2.168 \text{ k}\Omega$

Since X_C and X_L are equal, along with being 180° out of phase, the net reactance is zero which makes the total impedance equal to the resistor $\therefore Z_T = R$

Find total current and voltages

- $I_T = \frac{V_{in}}{Z_T} = \frac{V_{in}}{R} = \frac{0.3535}{47} = 7.521\text{mA}$

Since this is a series circuit, the current found for the total will also be the current flowing through the reactive components.

- $V_C = (X_C)(I_T) = (2.168\text{k}\Omega)(7.521\text{mA}) = 16.306\text{V}$

- $V_L = (X_L)(I_T) = (2.168\text{k}\Omega)(7.521\text{mA}) = 16.306\text{V}$

As you can see, the resonant circuit appears to amplify the voltages.

Find the Q of the circuit


- $Q = \frac{X_L}{r_s} \rightarrow$ Since there is no value given for a resistance of the coil, we have to use the only resistance in the circuit to find this value

$$\therefore Q = \frac{X_L}{R} = \frac{2.168k\Omega}{47\Omega} = 46.128$$

Solve for Bandwidth and Cutoff frequencies

- $\Delta f = f_2 - f_1 = \frac{f_r}{Q} = \frac{73.142\text{kHz}}{46.128} = 1.592\text{kHz}$
→ This means the frequency will vary $\pm 796\text{Hz}$ ($\frac{\Delta f}{2}$). The entire range is also known as Bandwidth.
- $f_2 = f_r + \frac{\Delta f}{2} = 73.412\text{kHz} + 796\text{Hz} = 74.208\text{kHz}$
- $f_1 = f_r - \frac{\Delta f}{2} = 73.412\text{kHz} - 796\text{Hz} = 72.616\text{kHz}$
- $\theta = 0^\circ$ since X_L and X_C are canceling, which means at resonance the circuit is purely resistive.

Parallel Resonant circuit

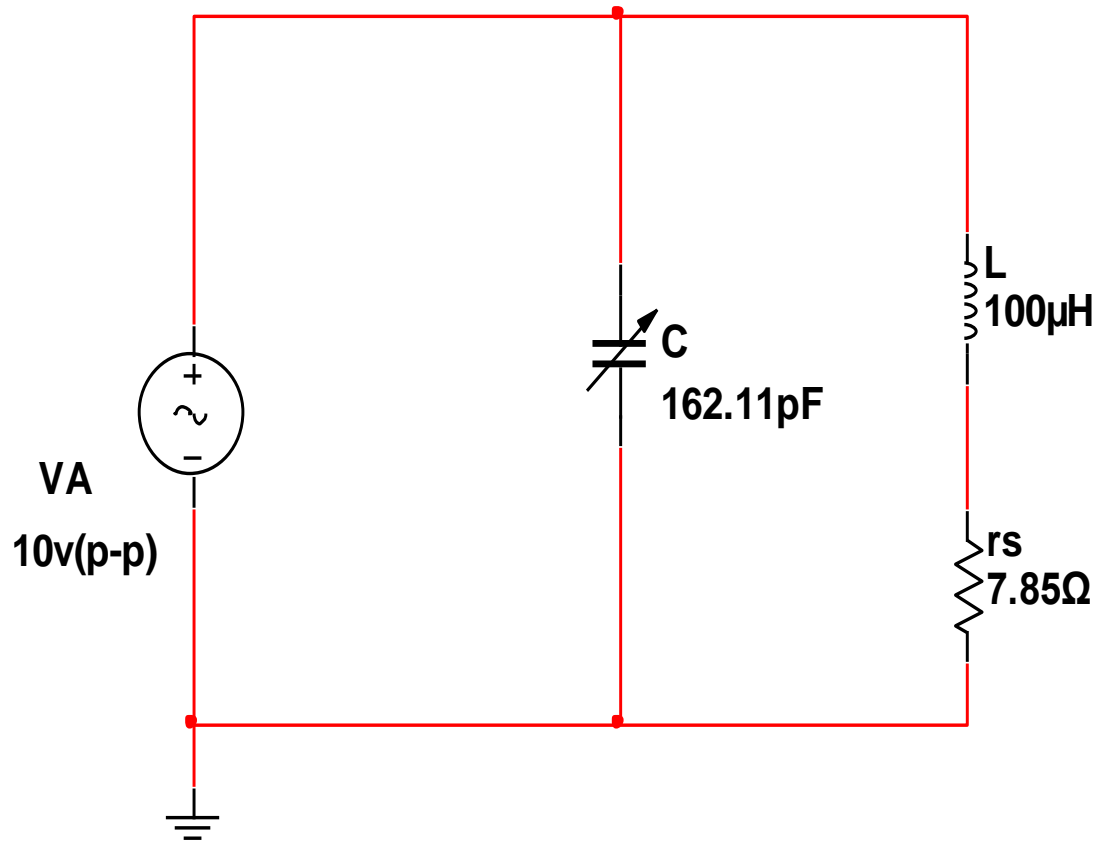

$$f_r = ?$$

$$I_L = ?$$

$$X_L = ?$$

$$Q = ?$$

$$X_C = ?$$

$$Z_{eq} = ?$$

$$I_C = ?$$

$$I_T = ?$$

$$\Delta f = ?$$

Solve for f_r

- $$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{6.28\sqrt{(100 \times 10^{-6})(162.11 \times 10^{-12})}} =$$
$$\frac{1}{6.28\sqrt{1.621 \times 10^{-14}}} = \frac{1}{799 \times 10^{-9}} = 1.25 \text{MHz}$$

Find the reactances

- $X_L = 2\pi fL = (6.28)(1.25 \times 10^6)(100 \times 10^{-6}) = 785.394\Omega$
- $X_C = \frac{1}{2\pi fC} = \frac{1}{(6.28)(1.25 \times 10^6)(162.11 \times 10^{-12})} = \frac{1}{1.273 \times 10^{-3}} = 785.417\Omega$

Since this is a parallel circuit, we presume the applied voltage will be across each reactive component.

Find branch currents and the equivalent impedance

- $I_C = \frac{V_A}{X_C} = \frac{10}{785.417} = 12.732\text{mA}$
- $I_L = \frac{V_A}{X_L} = \frac{10}{785.398} = 12.732\text{mA}$
- $Q = \frac{X_L}{r_s} = \frac{785.398}{7.85} = 100.051 \cong 100$
- $Z_{eq} = QX_L = (100.051)(785.398) = 78.58\text{k}\Omega \rightarrow$
Since this is the only way we are going to get the total impedance, we now need to use it to find the total current.

Find total current

- $I_T = \frac{V_A}{Z_{eq}} = \frac{10}{78.58k\Omega} = 127.259\mu A$

Again, we can see the magnification of the current due to resonance.

Solve for Bandwidth and Cutoff frequencies

- $\Delta f = f_2 - f_1 = \frac{f_r}{Q} = \frac{1.25\text{MHz}}{100.051} = 12.494\text{kHz}$

→ This means the frequency will vary

$\pm 6.247\text{kHz} \left(\frac{\Delta f}{2} \right)$

- $f_2 = f_r + \frac{\Delta f}{2} = 1.25\text{MHz} + 6.247\text{kHz} = 1.256\text{MHz}$

- $f_1 = f_r - \frac{\Delta f}{2} = 1.25\text{MHz} - 6.247\text{kHz} = 1.243\text{MHz}$